

Prelab 2

Jaiden Gann

June 8, 2022

Part 1: inverting op-amp

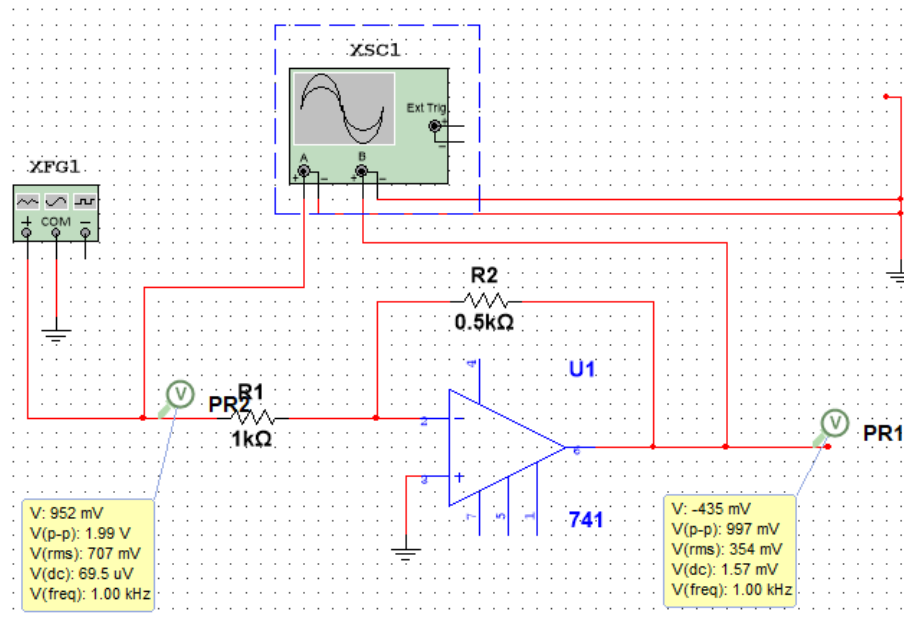


Figure 1. Inverting op-amp circuit diagram

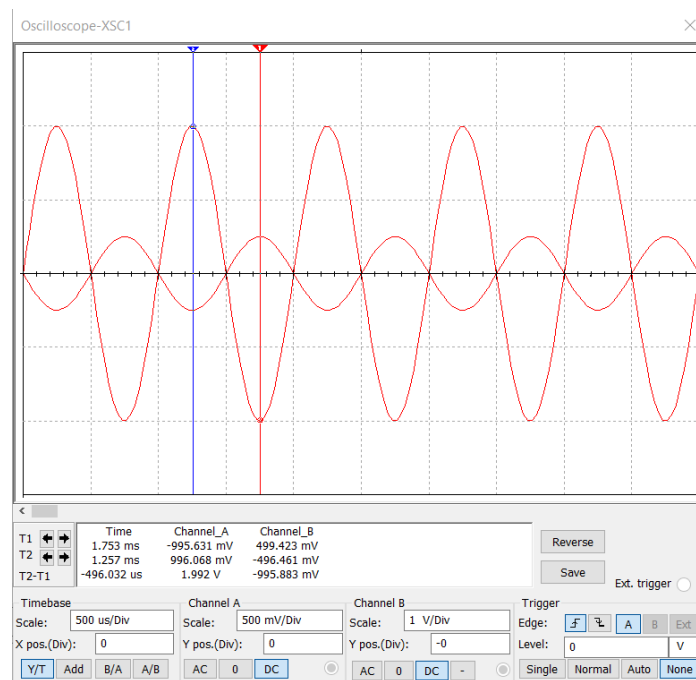


Figure 2. Input and output waveforms for Figure 1

Table 1. Simulation results for inverting op-amp

| $V_{INpp}(V)$ | $R_{IN}(k\Omega)$ | $R_F(k\Omega)$ | $V_{OUTpp}(V)$ O-Scope | Gain (v/v) | $V_{OUTrms}(V)$ DMM |
|---------------|-------------------|----------------|------------------------|------------|---------------------|
| 2 | 1 | 0.5 | 1.992 | 0.5 | 0.354 |
| | | 1 | 1.993 | 1 | 0.707 |
| | | 2 | 1.993 | 2.079 | 1.47 |
| | | 3 | 1.992 | 2.26 | 1.60 |
| | | 4 | 1.991 | 2.51 | 1.78 |

Part 2:non-inverting op-amp

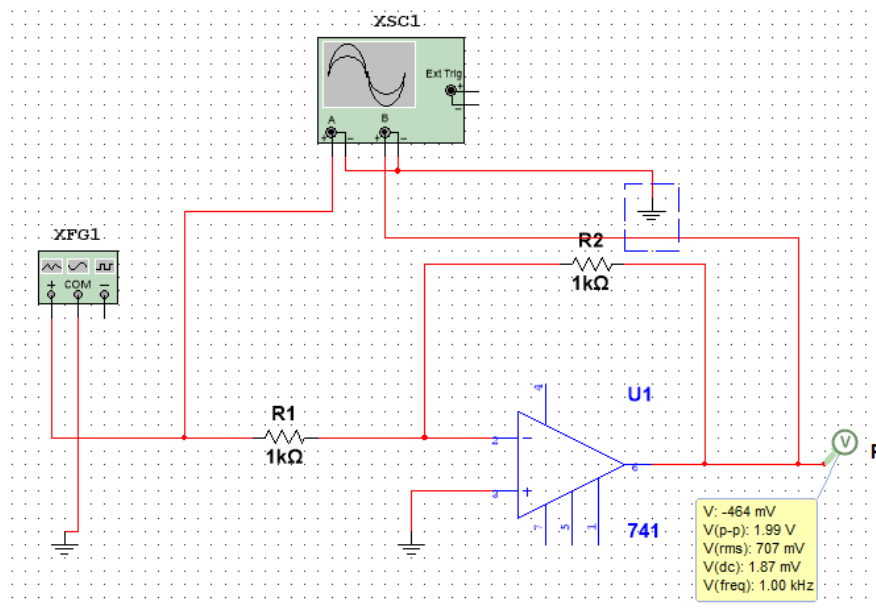


Figure 3. Non-inverting op-amp circuit diagram

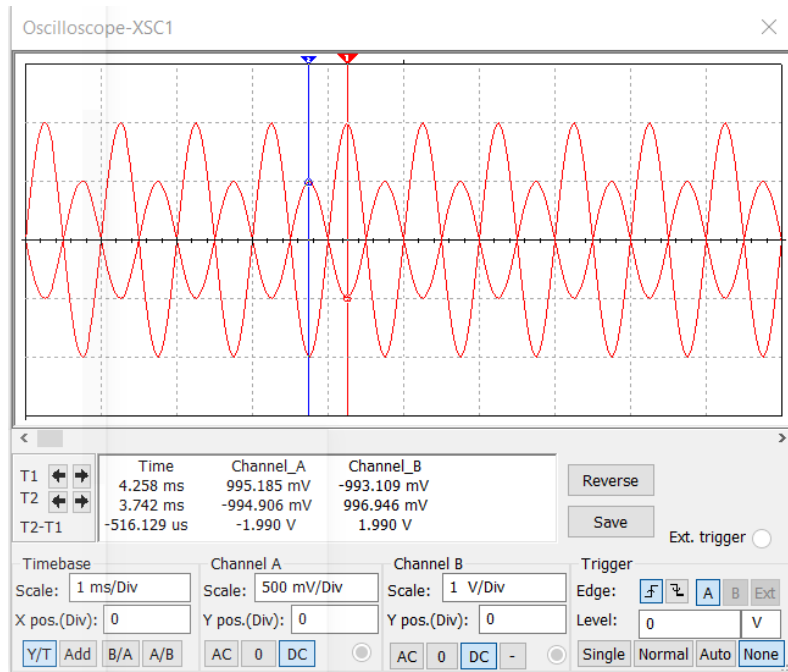


Figure 4. Input and output waveforms for Figure 3

Table 2. Simulation results for non-inverting op-amp

| $V_{INpp}(V)$ | $R_{IN}(k\Omega)$ | $R_F(k\Omega)$ | $V_{OUTpp}(V)$ O-Scope | Gain (v/v) | $V_{OUTrms}(V)$ DMM |
|---------------|-------------------|----------------|------------------------|------------|---------------------|
| 2 | 1 | 0.5 | 1.991 | 0.5 | 0.354 |
| | | 1 | 1.990 | 1 | 0.707 |
| | | 2 | 1.990 | 2.12 | 1.50 |
| | | 3 | 1.993 | 2.33 | 1.63 |
| | | 4 | 1.989 | 2.51 | 1.78 |

The numbers I got for V_{OUTpp} seem wrong to me for both non-inverting and inverting and am not sure I measured it correctly.